

## Boolean Algebra

- **Boolean algebra**
  - Boolean operations
  - Laws and identities of Boolean algebra
  - Simplifying Boolean expressions
- **Switching Algebra**
  - Logic gates
  - Designing logic circuits

Slide 1

## Boolean Algebra

- A **Boolean algebra** is a **set**  $B = \{a, b, \dots\}$  and the **binary operators**  $+$  and  $\cdot$ , together with the **unary operator**  $'$ , that satisfies the following:
  - **Axiom 1 Closure**
    - ◆  $a+b, a \cdot b, a' \in B$
  - **Axiom 2 Commutative Law**
    - ◆  $a+b = b+a$
    - ◆  $a \cdot b = b \cdot a$
  - **Axiom 3 Distributive Law**
    - ◆  $a \cdot (b + c) = a \cdot b + a \cdot c$
    - ◆  $a + (b \cdot c) = (a + b) \cdot (a + c)$

Slide 2

## Boolean Algebra

- A **Boolean algebra** is a **set**  $B = \{a, b, \dots\}$  and the **binary operators**  $+$  and  $\cdot$ , together with the **unary operator**  $'$ , that satisfies the following:
  - **Axiom 4 Identity Law**
    - ◆  $a+0 = a$
    - ◆  $a \cdot 1 = a$  where 0 and 1 are distinct and unique
  - **Axiom 5 Complementary Law**
    - ◆  $a+a' = 1$  where  $a'$  is unique
    - ◆  $a \cdot a' = 0$

Slide 3

## Boolean Algebra

- **Boolean operations**
  - **Boolean complement ( $'$ )**
    - ◆  $0' = 1$
    - ◆  $1' = 0$
  - **Boolean sum ( $+$ )**
    - ◆  $0+0 = 0$
    - ◆  $0+1 = 1$
    - ◆  $1+0 = 1$
    - ◆  $1+1 = 1$
  - **Boolean product ( $\cdot$ )**
    - ◆  $0 \cdot 0 = 0$
    - ◆  $0 \cdot 1 = 0$
    - ◆  $1 \cdot 0 = 0$
    - ◆  $1 \cdot 1 = 1$

Slide 4

## Boolean Algebra

- **Laws of Boolean Algebra**
  - Theorem 1: **Associative**
    - ◆  $a + (b + c) = (a + b) + c$
    - ◆  $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
  - Theorem 2: **Idempotency**
    - ◆  $a+a = a$
    - ◆  $a \cdot a = a$
  - Theorem 3: **Dominance**
    - ◆  $a+1=1$
    - ◆  $a \cdot 0 = 0$

Slide 5

## Boolean Algebra

- **Laws of Boolean Algebra**
  - Theorem 4: **Double Complement**
    - ◆  $(a')' = a$
  - Theorem 5: **Absorption**
    - ◆  $a + a \cdot b = a$
    - ◆  $a \cdot (a + b) = a$
  - Theorem 6: **De Morgan's**
    - ◆  $(a+b)' = a' \cdot b'$
    - ◆  $(a \cdot b)' = (a' + b')$

Slide 6

## Boolean Algebra

### Identities:

- Identity 1:  $a(a' + b)$
- Identity 2:  $a + a'b = a + b$
- Identity 3:  $ab(a + b) = ab$
- Identity 4:  $(ab)'(a + b) = ab' + a'b$
- Identity 5:  $(ab' + a'b')' = ab + a'b$
- Identity 6:  $(a + b)(b + c)(a + c) = ab + bc + ac$
- Identity 7:  $(a + b)(a' + c) = ac + a'b$
- Identity 8:  $ac + ab + bc' = ac + bc'$
- Identity 9:  $(a + b)(b + c)(a' + c) = (a + b)(a' + c)$

Slide 7

## Boolean Algebra

- If an algebra A is a **Boolean algebra**, then we can summarize this as

$$A = (B = \{a, b, \dots\}; +, \cdot, ' ; 0, 1)$$

### Examples:

- Set algebra:  $(P(U); \cup, \cap, ' ; \emptyset, U)$
- Logic:  $(B, \vee, \wedge, ', \text{False}, \text{True})$   
where B is a set of propositions.

Slide 8

## Boolean Algebra

- The **dual** of a statement involving Boolean expressions is obtained by replacing:

- 0 with 1
- + with  $\cdot$
- 1 with 0
- $\cdot$  with +

### Examples:

What is the dual of each of the following?

- $(a + b)' = a'b'$
- $(x+y)(x+1) = x + xy + y$

Slide 9

## Boolean Algebra

### The Duality Principle

The dual of a theorem in Boolean algebra is also a theorem.

### Hierarchy of Boolean Operators

(highest to lowest)  $' , \cdot , +$

### Simplifying Boolean Expressions

- Reduce a Boolean expression into one that uses the minimal number of operations
  - ◆ Apply axioms, theorems and identities
- Important step in designing logic circuits

Slide 10

## Boolean Algebra

### Simplifying Boolean Expressions

#### Example:

Simplify the expression  $ab + a'b + ab'$ .

Solution:

$$ab + a'b + ab'$$

$$= b + a$$

Slide 11

## Boolean Algebra

### Simplifying Boolean Expressions

#### Example:

Simplify the expression  $ab + a'c + bcd$ .

Solution:

$$ab + a'c + bcd$$

$$= ab + a'c$$

Slide 12

## Boolean Algebra

### Other examples/exercises:

- 1)  $[(a + b') + c(a + b')]$
- 2)  $a'b' + ab + a'b$
- 3)  $(a + b')(a' + b')$
- 4)  $ab + (b'd)' + (c + d')$
- 5)  $ab + (a + b)c' + b$
- 6)  $a + b(a' + b + c)'$
- 7)  $cd + ab + d + [ad(bc + ad)]$

Slide 13

## Switching Algebra

- A **switching function** is a *binary-valued* function of one or more binary-valued variables.
- Given  $x_1, x_2, \dots, x_n$  where  $x_i = 0$  or  $1$  then the switching function  $S$  is defined as  

$$S: (x_1 \times x_2 \times \dots \times x_n) \rightarrow \{0,1\}$$

### Example:

Define switching function  $f(x,y,z) = xy + (y'z)'$ .  
 What is  $f(x,y,z)$  when  $x, y = 0$  and  $z = 1$ ?  
 $f(0,0,1)$

Slide 14


## Switching Algebra

### Basic Gates

#### AND gate

Truth table:


a	b	$a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

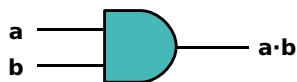

#### OR gate

Truth table:

a	b	$a + b$
0	0	0
0	1	1
1	0	1
1	1	1

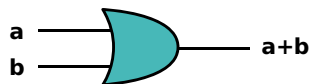

Slide 15

## Switching Algebra

### Basic Gates (cont'd)

#### NOT gate

Truth table:

a	$a'$
0	1
1	0



Slide 16


## Switching Algebra

### Other Gates

#### NAND (not AND) gate

Truth table:


a	b	$a b$
0	0	1
0	1	1
1	0	1
1	1	0

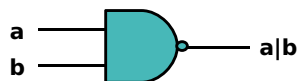

#### NOR (not OR) gate

Truth table:

a	b	$a  b$
0	0	1
0	1	0
1	0	0
1	1	0

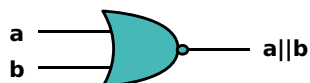

Slide 17


## Switching Algebra

### Other Gates (cont'd)


#### XOR (Exclusive OR) gate

Truth table:

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

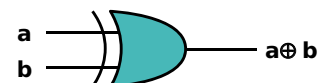

Note:  $a \oplus b = a'b + ab'$

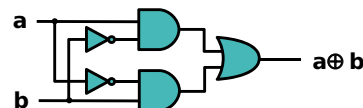

Slide 18

## Switching Algebra

### Examples:

- Draw the combinational circuit for  
 $\diamond f(a,b,c) = a + (bc)'$

$\diamond f(a,b) = a' + ab' + b$

Slide 19

## Designing Logic Circuits

### CASE 1: Given: Switching function

- Step 1: Simplify the function.
- Step 2: Draw the corresponding logic diagram

### Examples/Exercises:

Design logic circuits for the following switching f'ns.

- $f(x,y) = x'y' + xy + x'y$ .
- $f(x,y) = x' + y'$ .
- $f(x,y,z) = (xy + z)'$ .
- $f(a,b) = (a + b)'(a' + b')$ .
- $f(a,b,c) = ab + bc(b + c)$ .
- $f(a,b,c) = a + b(a + c) + ac$ .


Slide 20

## Designing Logic Circuits

### Example:

Design a logic circuit for  $f(x,y) = x'y' + xy + x'y$

Note that this switching function has the following corresponding logic diagram:

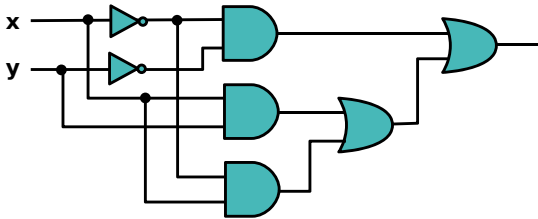

Slide 21

## Designing Logic Circuits

### Example:

Design a logic circuit for  $f(x,y) = x'y' + xy + x'y$

Solution:

### Step 1: Simplify switching function

$$x'y' + xy + x'y$$

$$= x' + y$$

Slide 22

## Designing Logic Circuits

### Example:

Design a logic circuit for  $f(x,y) = x'y' + xy + x'y$

Solution:

### Step 2: Draw logic diagram

$$\text{Since } x'y' + xy + x'y = x' + y$$

Slide 23

## Designing Logic Circuits

### CASE 2: Given: general description of the switching function

- Step 1: **Tabulate** the function for all possible input values based on the description of the function.
  - For each output =1, write a conjunct of all input variables  $x_i$  such that
    - if  $x_i = 0$ , use  $x_i'$
    - if  $x_i = 1$ , use  $x_i$
- Step 2: **Connect** all the conjuncts obtained in the previous step as disjuncts.
- Step 3: **Simplify** the expression if possible.
- Step 4: **Draw** the corresponding logic diagram.

Slide 24

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**
  - ◆ *Input*: accepts three bits
  - ◆ *Output*: if majority of the input bits are equal to 1, then the function returns a 1.
- We may define the majority function M thus:

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

Slide 25

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

#### Step 1: Tabulate the function ...

a	b	c	M(a,b,c)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Slide 26

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

#### Step 1: ... and write a conjunct whenever output = 1

a	b	c	M(a,b,c)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Slide 27

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

#### Step 2: Connect the conjuncts as disjuncts

a	b	c	M(a,b,c)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Slide 28

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

#### Step 3: Simplify the expression ...

$$a'bc + ab'c + abc' + abc$$

$$= bc + a(b \oplus c)$$

Slide 29

## Designing Logic Circuits

### ● Example:

- Design a logic circuit for the **majority function**

$$M(a, b, c) = \begin{cases} 1 & \text{if at least two of } a, b, c \text{ are 1} \\ 0 & \text{otherwise} \end{cases}$$

#### Step 4: Draw the corresponding logic diagram.

$$bc + a(b \oplus c)$$

Slide 30

## UP NEXT on CMSC 56 ...

### ● Read up on ...

#### ■ Matrix/Linear Algebra

- ◆ What is a **matrix**?
- ◆ What is a **square matrix**?
- ◆ What is a **diagonal matrix**?
- ◆ What is a **scalar matrix**?
- ◆ How do you ...
  - **add** one matrix to another?
  - **multiply** a matrix by another?
  - get the **transpose** of a matrix
  - multiply a matrix by a **scalar**?